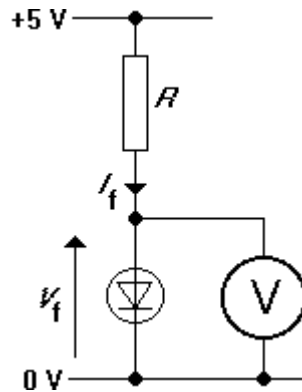


### Investigating the $I$ - $V$ characteristic of a diode

In the real world of electronics, the current in a component is often calculated from the voltage drop across a resistor in series with it. This is because it is usually not possible to break open a circuit to insert the ammeter!

1. Set up the circuit as shown, with  $4700\ \Omega$  for  $R$ . Use a 1N4148 signal diode.



2. Measure the forward voltage  $V_f$  of the diode. Calculate the forward current  $I_f$  using Ohm's Law applied to the resistor. (You should get about 0.7 V and just under 1 mA.)
3. Repeat steps 1 and 2 with the following values of  $R$ .

$2200\ \Omega$      $1000\ \Omega$      $470\ \Omega$      $220\ \Omega$      $100\ \Omega$

4. Use your results to plot a current–voltage graph for the diode. Use axes similar to the ones shown below.

